

**University of Bahrain**  
**College of Information technology**  
**Department of Computer Engineering**

**Test (2)**

Student Name
I.D. No.
Section

**Course Title:** Digital Logic

**Course number:** ITCE 250

**Semester:** 1

**Academic Year:** 2015/2016

**Duration :** 1 hour

**Date:** 9<sup>th</sup> December 2015

**Read the following before you start:**

1. Write your name, ID and section number
2. Answer all questions.
3. Write your answers on the attached sheets only

4. **Use PEN only**

4- Use PEN only

Question	Mark	Mark attained
1	16	16
2	16	16
3	16	16
4	16	16
5	16	16
Total	80	80

**Question [1]: [16 mark]**

Realize the following function as a minimum two-level NAND gate circuit.



$$f(A, B, C, D) = \prod M(0, 1, 7, 9, 10, 13) \cdot \prod D(2, 6, 14, 15)$$

$f(A, B, C, D) = \sum m(3, 4, 5, 8, 11, 12) + \sum d(2, 6, 14, 15)$


AB \ CD	00	01	11	10
00	0	1	1	1
01	0	1	0	0
11	1	0	X	1
10	X	X	X	0

$\overline{A}B\overline{C}$  (points to minterms 01, 11, 10 in row 00)  
 $A\overline{C}\overline{D}$  (points to minterms 00, 01, 11 in column 00)  
 $\overline{B}CD$  (points to minterms 01, 11 in column 01)
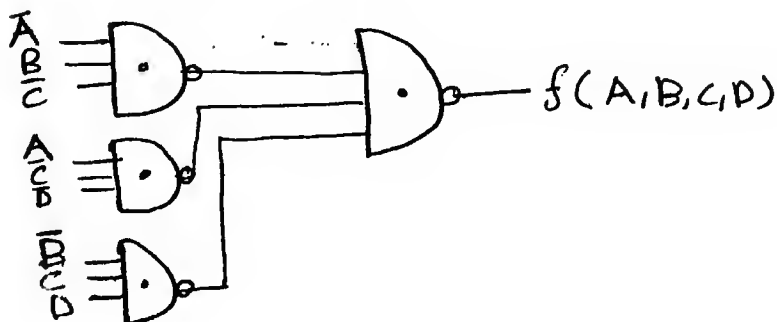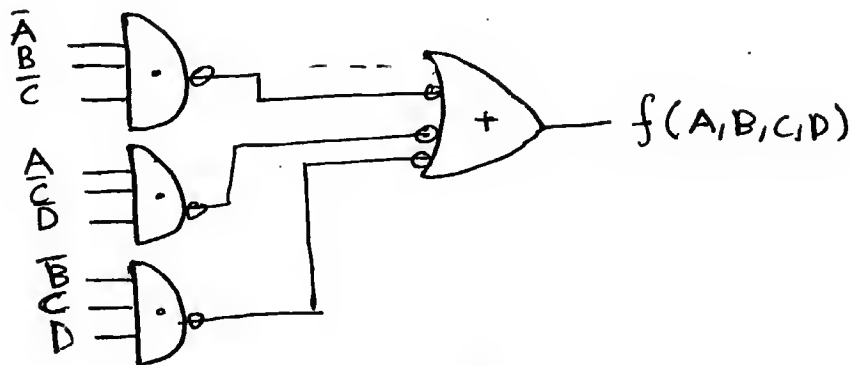
$$f = \overline{A}B\overline{C} + A\overline{C}\overline{D} + \overline{B}CD$$



Question [2]: [ 16 Marks]

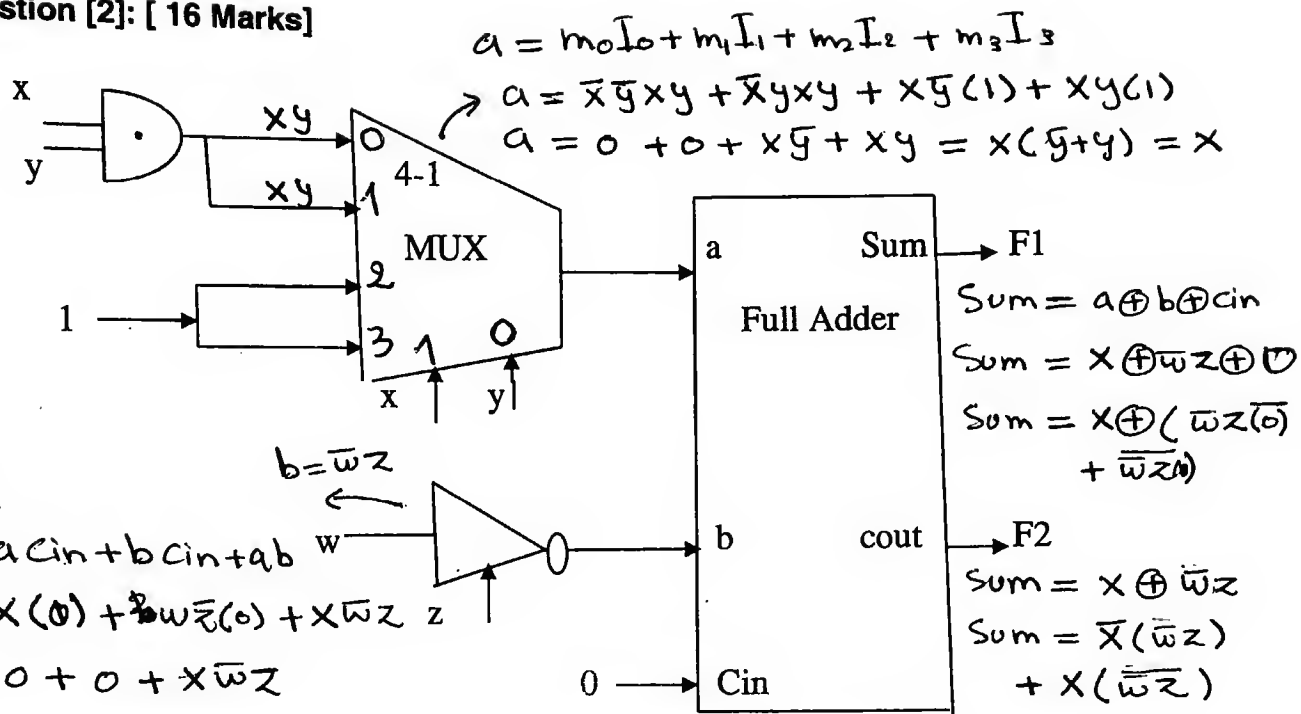

1- Derive the truth table and output equations of a Full-Adder.

2- Write the input equations of the given F-A.

3- Write the output equations of the given F-A as Sum of Products.

1)

a	b	cin	cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

cout	a	0	1
b	0	0	0
0	0	0	1
1	0	1	1
1	0	1	1

sum	a	0	1
b	0	0	1
0	1	0	1
1	0	1	0
1	1	0	0

no simplification

$$cout = a cin + ab + bcin$$

$$\begin{aligned}
 Sum &= \bar{a}\bar{b}cin + \bar{a}b\bar{c}in + \bar{a}b\bar{c}in + a\bar{b}cin \\
 &= \bar{a}(b\bar{c}in + b\bar{c}in) + a(\bar{b}cin + bcin) \\
 &= \bar{a}(b \oplus cin) + a(\bar{b} \oplus cin) \\
 &= a \oplus (b \oplus cin) = a \oplus b \oplus cin
 \end{aligned}$$

2)  $a = x$  ,  $b = \bar{w}z$  ,  $cin = 0$

3)  $F_1 = \bar{x}\bar{w}z + x(w + \bar{z}) = \bar{x}\bar{w}z + xw + x\bar{z}$


$F_2 = x\bar{w}z$

**Question [3] : [16 marks]**

- a- Implement the function  $F$  with a 3-to-8 active high decoder and NOR extra gate.


$$F(a,b,c) = \sum m(0,2,3,5,7)$$

$$F(a,b,c) = \prod(1,4,6)$$

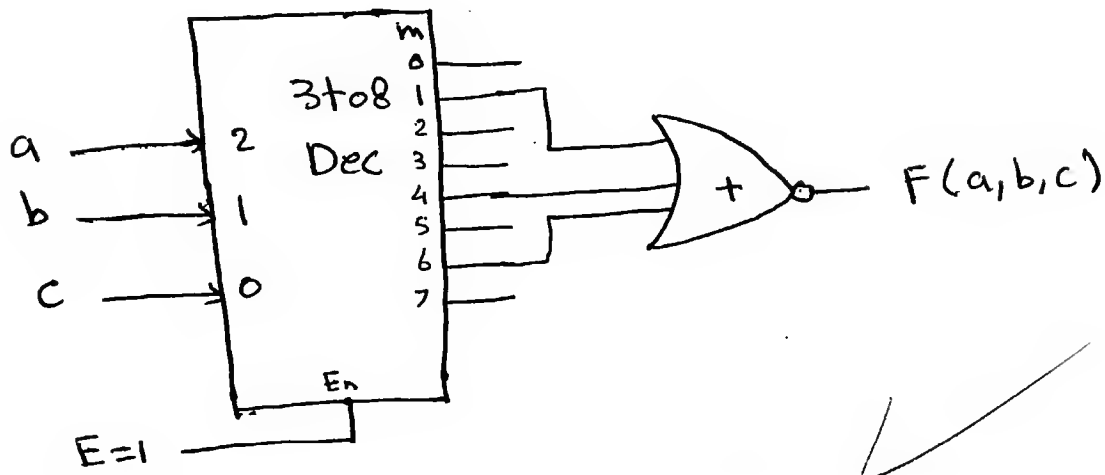

- b- Implement the same function  $F$  with 2-to-4 decoders and an OR gate.

$$F(a,b,c) = \sum m(0,2,3,5,7)$$

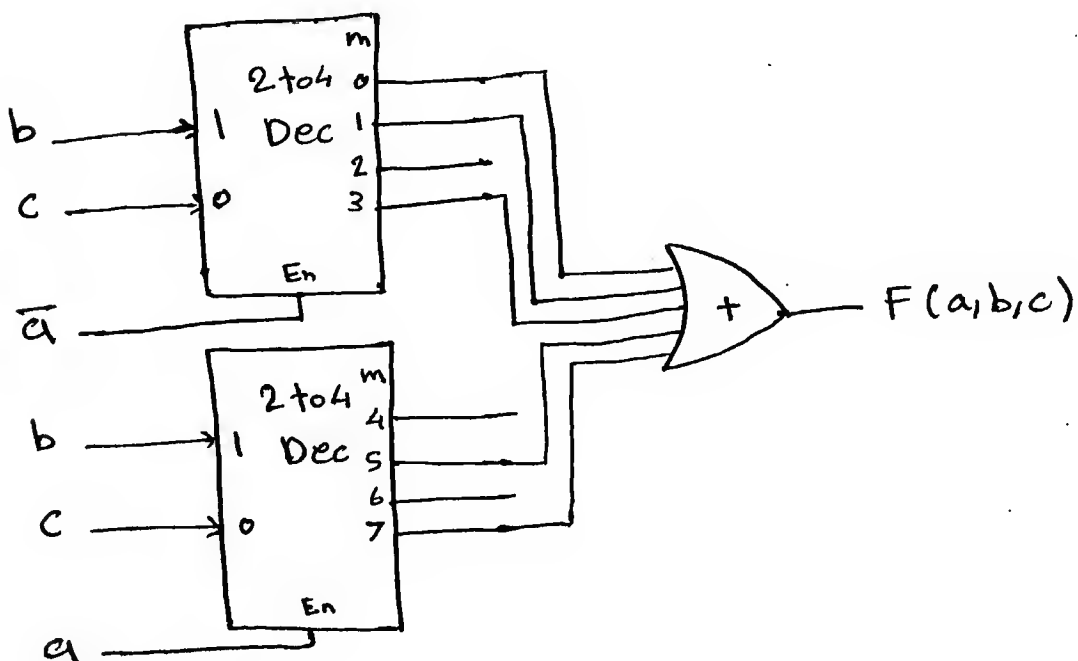

**Question [4] : [16 marks]**

A ROM is used to store the values of the word  $Y$ . Where  $Y$  is equal to:  
 $Y = X^2$   $X$  is a 3-bit number.

a- Give the ROM size in bits.

b- Draw the ROM structure by showing only the last line of the matrix array.

a)

$$Y_{\max} = (7^2)_{10} = (49)_{10}$$


$$X_{\max} = (111)_2 = (7)_{10}$$

$$(49)_{10} = (110001)_2$$


$$32 + 16 = 48$$

$$n = 3$$

$$m = 6$$

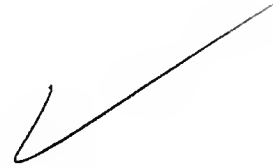
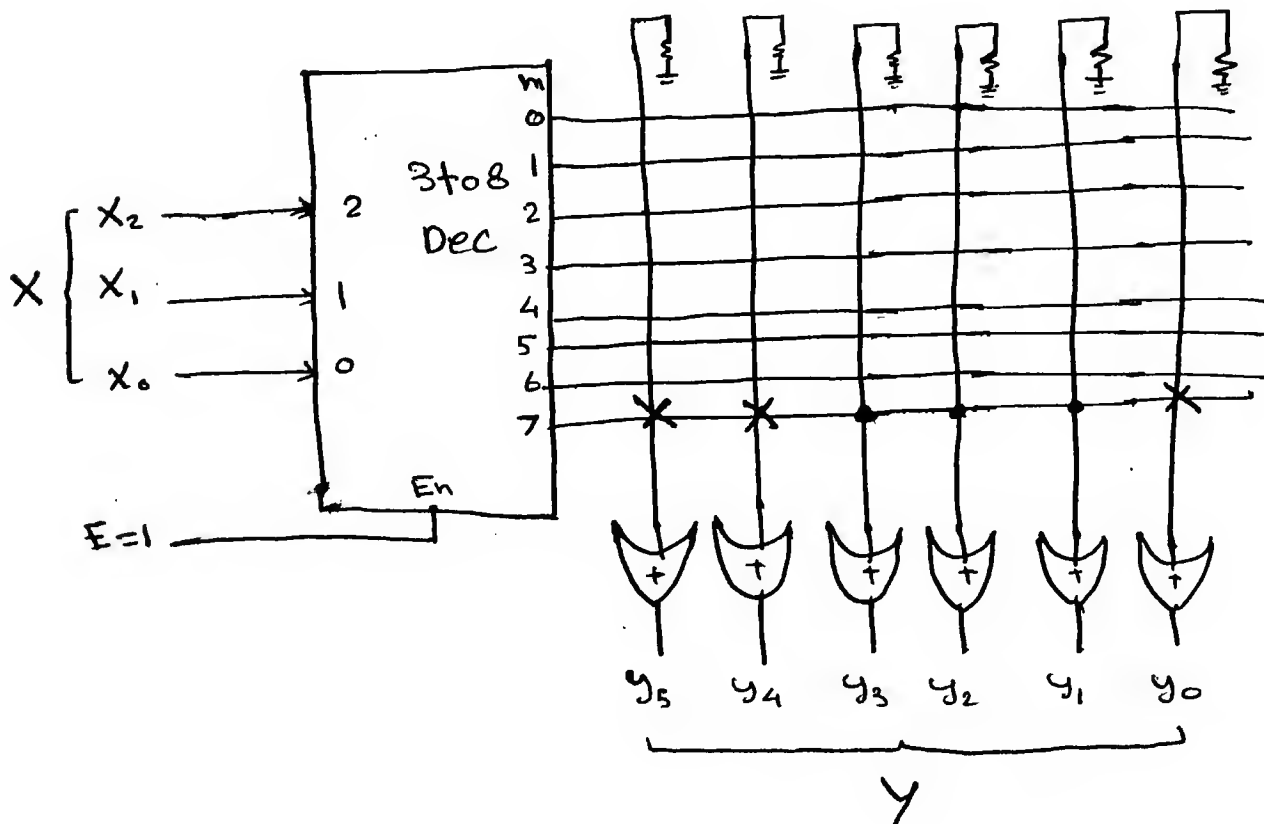
$$\text{ROM size} = 2^3 \times 6 = 8 \times 6 \Rightarrow 8 \text{ words} \times 6 \text{ bits}$$



**Question [5] : [16 marks]**

Complete the following timing diagram for a J-K flip-flop shown in the figure. Label the different states of Q as one of the following (Set, Reset, PreN, ClrN, no Q change, Q change). Assume initial value Q=0.

